

LISTA DE EXERCÍCIOS

TBJ - 02

1) Dado o circuito a seguir, determine: $A_i = \frac{i_A}{i_i}$, $A_v = \frac{v_o}{v_i}$,

$Z_i = \frac{v_i}{i_i}$, $Z_o = \frac{v_o}{i_o}$, sendo $h_{ie} = 1k\Omega$, $h_{re} = 2 \cdot 10^{-4}$, $h_{fe} = 50$,

$h_{oe} = 20\mu$.


RTA:

$$A_i = 47,84$$

$$A_v = -38,04$$


$$Z_i = 975,98$$

$$Z_o = 1960,78$$

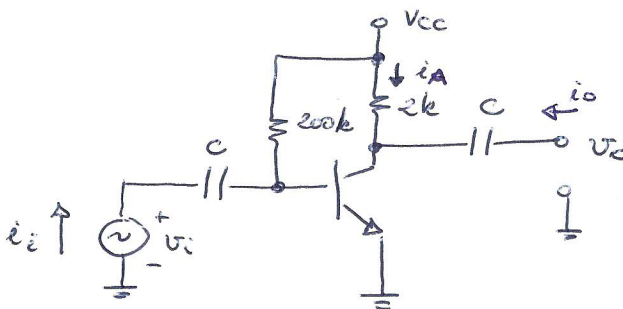

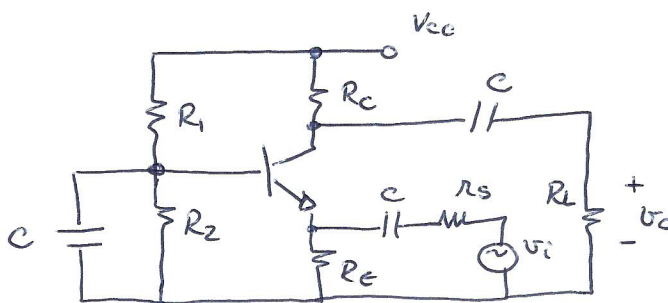
2) Determine $A_v = \frac{v_o}{v_i}$

RTA: $A_v = +\frac{h_{fe}}{h_{ie}} (R_c \parallel R_L)$




3) Determine: $A_v = \frac{v_o}{v_i}$, Z_o , Z_i , onde $\beta_1 = 140$, $\beta_2 = 180$,

$h_{ie1} = 5,8k$, $h_{ie2} = 42$

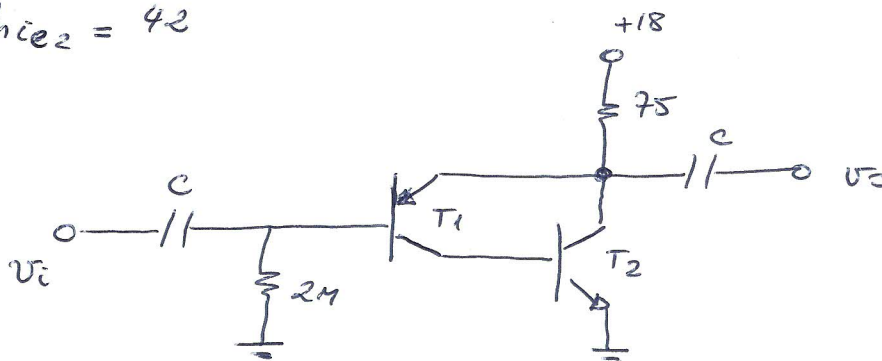

4) Determine: A_v , Z_o , Z_i

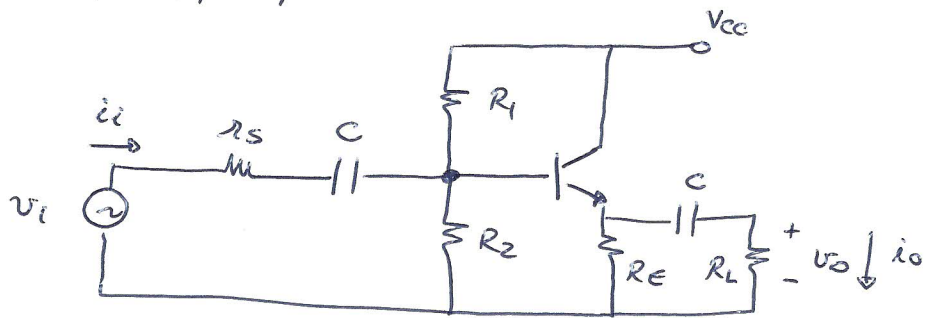


$$R_{in} : A_v = \frac{v_o}{v_i} = \frac{r_s \parallel R_B}{r_s} \left[1 - \frac{r_s \parallel R_B + h_{ie}}{\frac{R_E R_L}{R_E + R_L} h_{fe} + (r_s \parallel R_B) + h_{ie} + R_E \parallel R_L} \right]$$


$$\text{onde } R_B = R_1 \parallel R_2$$

$$Z_o = \frac{(h_{fe} + 1) R_E + h_{ie} + R_T}{R_E (h_{ie} + R_T)} \quad \text{onde } R_T = r_s \parallel R_1 \parallel R_2$$

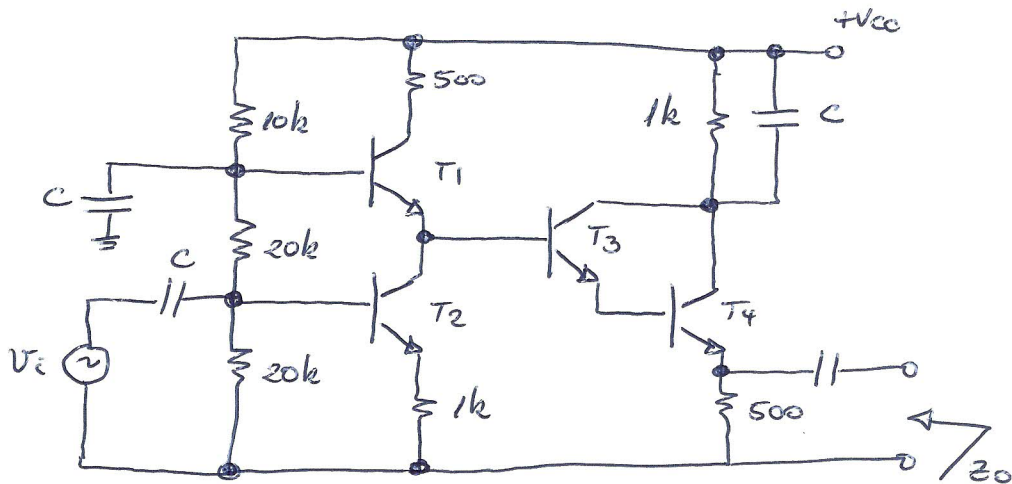5) Determine Z_o , sendo $h_{ie1} = 1k$, $h_{ie2} = 2k$, $h_{ie3} = 1,5k$,
 $h_{ie4} = 2k$, $h_{fe} = 50$



6)

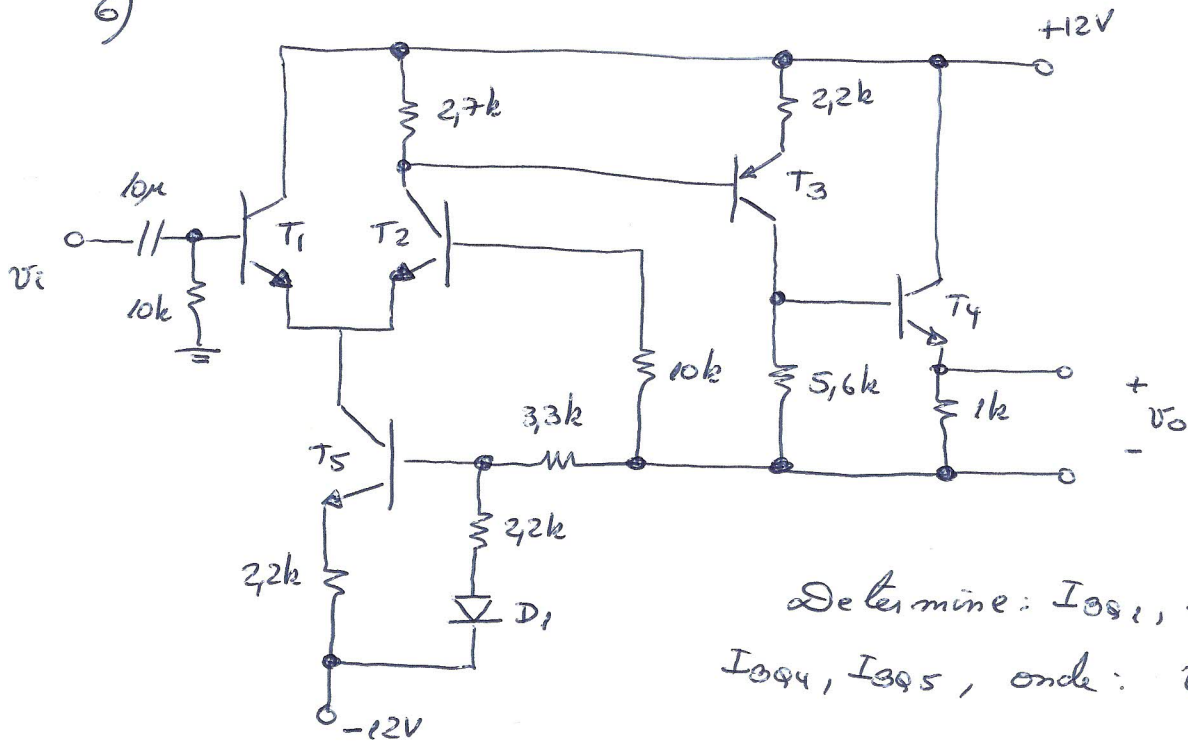

Determine: $I_{BQ1}, I_{BQ2}, I_{BQ3},$
 I_{BQ4}, I_{BQ5} , onde: $V_{BEi} = V_D = (\pm) 0,7$
 e $\beta_i = 200$ para $i = 1, 2, \dots, 5$